

## High Fidelity Receiver Modification for the Cobra 148 and Uniden Grant XL

With very little effort, the receiver section can be modified to vastly improve the sound quality. The modification below involves replacing a few capacitors and expands the range in both the lower and upper audio frequency ranges. The values shown in the red boxes are the new values. Use ceramic capacitor. **DO NOT USE ELECTROLYTICS!**

